

Analog IC Design – Cadence Tools

Lab 03

Cascode Amplifier

Part 1: Sizing Chart

Use $V^* = 200 \text{ mV}$ and $I_D = 20 \text{ uA}$. Use $V_{DD} = 1.8 \text{ V}$

For a square-law device, $V^* = V_{ov}$, however, for a real MOSFET they are not equal.

The lower the V^* the higher the gain, but the larger the area and the lower the speed.

$$g_m = 2 \cdot I_D / V^* = (2 \cdot 20 \cdot 10^{-6}) / 200 \cdot 10^{-3} = 200 \mu$$

$$V_{ov} = V_{GS} - V_{TH}$$

1. We use $V_{DS} = V_{DD}/2 = 3/2 = 1.5 \text{ V}$, $g_m/I_D = 10 \text{ S/A}$
 $A_v = g_m r_o = 50$, $I_B = 20 \mu\text{A}$

ID	20u
gm/ID	10
gm/gds	50
VDS	0.9
VSB	0

Results:

Name	TT-27.0
1 ID	20u
2 IG	N/A
3 L	330n
4 W	3.32u
5 VGS	793.1m
6 VDS	900m


ID	20u
W	3.32u
L	330n
VDS	0.45
VSB	0.45

Results:

Name	TT-27.0
1 ID	20u
2 IG	N/A
3 L	330n
4 W	3.32u
5 VGS	909.8m
6 VDS	450m

$$V_{GS1} = 793.1 \text{ mV} \quad V_{GS2} = 909.8 \text{ mV} \quad V_B \text{ to set } V_{DS1} \approx V_{DS2} \approx 0.45 \text{ V}$$
$$V_B = V_{GS2} + V_{DS1} = 909.8 \text{ mV} + 0.45 \text{ V} = 1.3598 \text{ V}$$


find L3.

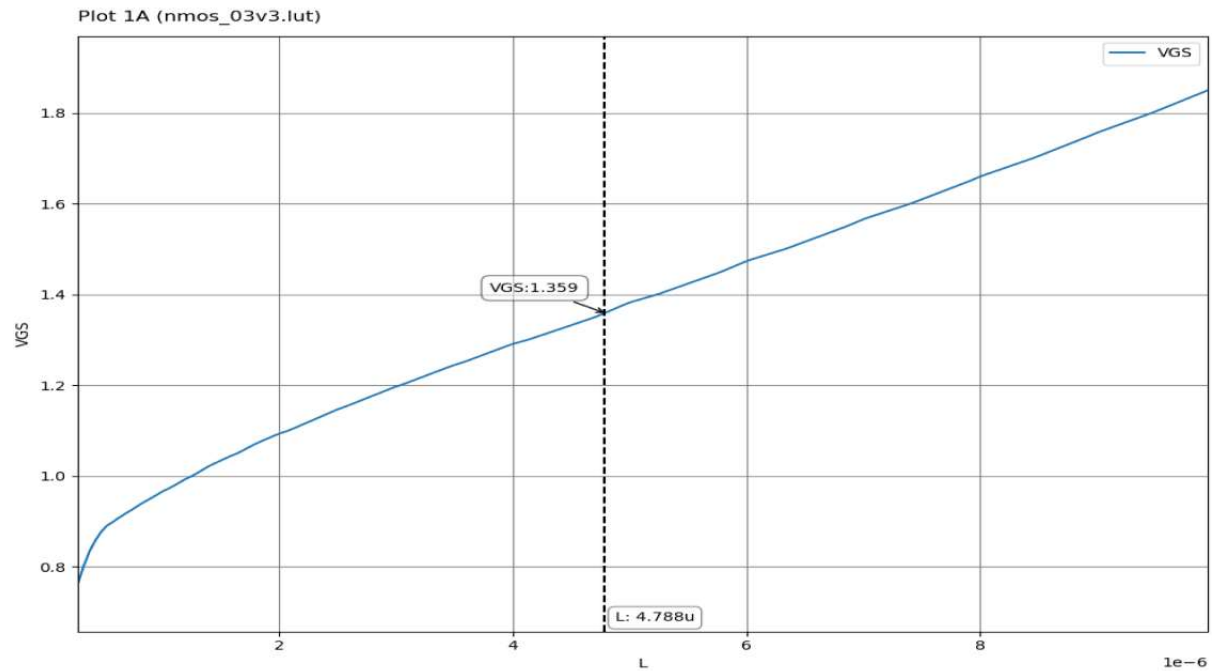

$L3 = 4.788\mu$ w is constant in all transistors

$V_{out1} = 0.9$ $0.9 - v_{gs1} = 0.9 - 793.1m = 0.1$

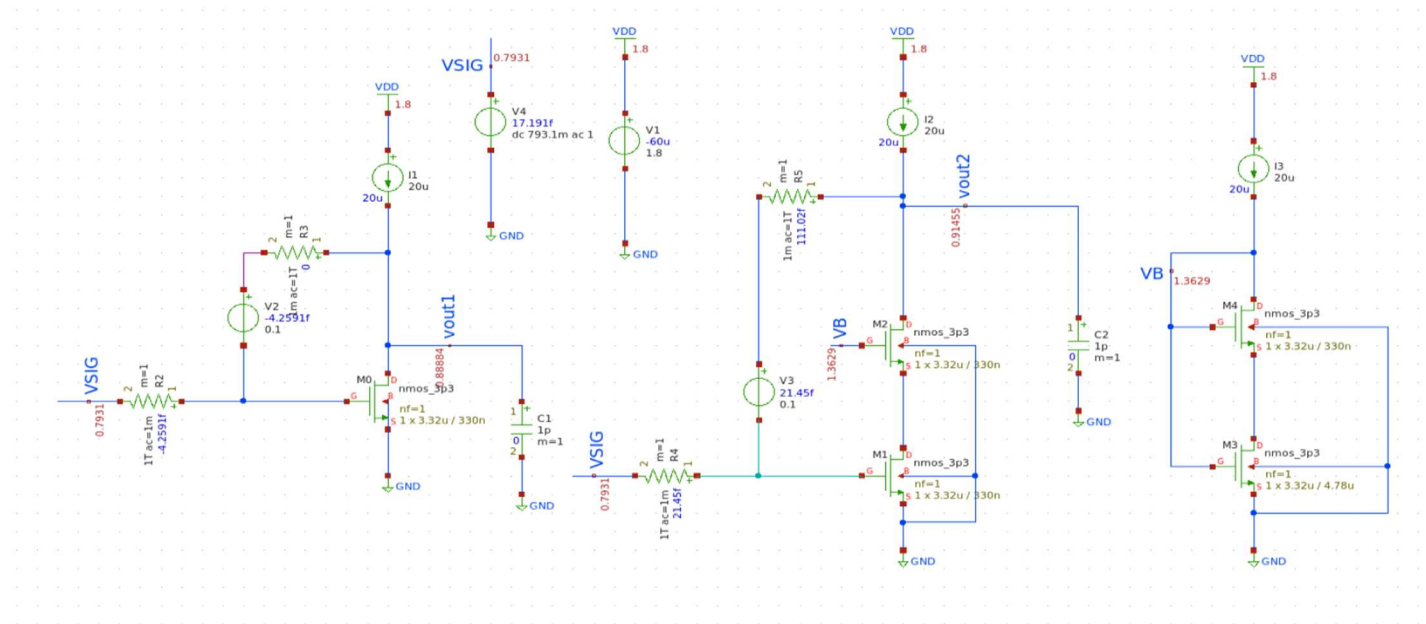$V_{out2} = 0.9$ $0.9 - v_{gs1} = 0.9 - 793.1m = 0.1$



Put the OP of all transistors in a table with the appropriate units

```

No. of Data Rows : 1
igain0 = 4.697477e+01
igain1 = 1.470747e+03
binary raw file "lab3.raw"
BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m.xm4.m0      m.xm2.m0      m.xm1.m0
  model      nmos_3p3.8      nmos_3p3.8      nmos_3p3.8
  id          2e-05          2e-05          2e-05
  vgs         0.90218        0.915022       0.814542
  vds         0.902172       0.4667         0.44782
  vth         0.773009       0.780565       0.682219
  vdsat       0.164456       0.167975       0.164748
  gm          0.000198406     0.000195565    0.000195901
  gds         4.5533e-06       5.70778e-06     5.51981e-06
  gmbs        4.09662e-05     4.09682e-05     5.35256e-05
  cdb         -1.99264e-16           -2.05429e-16    -2.67635e-16
  cgd         2.53027e-17       2.06986e-17     1.42304e-17
  cgs         -2.36966e-15       -2.39504e-15    -2.34144e-15
  csb         -2.98496e-16           -3.05899e-16    -3.9823e-16

BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m.xm0.m0      m.xm3.m0
  model      nmos_3p3.8      nmos_3p3.10
  id          2e-05          2e-05
  vgs         0.788833        1.36286
  vds         0.888826        0.460663
  vth         0.662441        0.656113
  vdsat       0.16076         0.548263
  gm          0.000199102     4.5917e-05
  gds         4.2385e-06       1.26435e-05
  gmbs        5.40445e-05     1.77984e-05
  cdb         -2.61442e-16           -8.1538e-15
  cgd         1.93885e-17       -4.44422e-15
  cgs         -2.31164e-15       -4.47538e-14
  csb         -3.91625e-16           -1.07572e-14

```

Parameters of M0, M1, M2, M3, M4

Parameters M0	Parameters M1	Parameters M2	Parameters M3	Parameters M4
Id= 2e-05	Id= 2e-05	Id= 2e-05	Id= 2e-05	Id= 2e-05
vgs= 0.7888	vgs= 0.8145	vgs= 0.915	vgs= 1.363	vgs= 0.9022
vds= 0.8888	vds= 0.4478	vds= 0.4667	vds= 0.4607	vds= 0.9022
vth= 0.6624	vth= 0.6822	vth= 0.7806	vth= 0.6561	vth= 0.773
vdsat= 0.1608	vdsat= 0.1647	vdsat= 0.168	vdsat= 0.5483	vdsat= 0.1645
gm= 0.0001991	gm= 0.0001959	gm= 0.0001956	gm= 4.592e-05	gm= 0.0001984
gds= 4.238e-06	gds= 5.52e-06	gds= 5.708e-06	gds= 1.264e-05	gds= 4.553e-06
gmbs= 5.404e-05	gmbs= 5.353e-05	gmbs= 4.097e-05	gmbs= 1.78e-05	gmbs= 4.097e-05

Check that all transistors operate in saturation. Does any transistor operate in triode? Why?

in simulation outputs,

All transistors operate in saturation as

But M3 not saturation the transistor operate in triode

As the transistor is vov increased to provide L and the ID is constant.

Do all transistors have the same v_{th} ? Why?

No, $M_4 > M_1 > M_2 > M_3 > M_0$

It is reduced due to DIBL effect Higher V_{TH} because it influences the body because Source voltage.

What is the relation ($\ll, <, =, >, \gg$) between g_m and g_{ds} ?

$g_m \gg g_{ds}$ to M_0 M_1 M_2 M_4

$g_m > g_{ds}$ to M_3

What is the relation ($\ll, <, =, >, \gg$) between g_m and g_{mb} ?

$g_m \gg g_{mb}$ to M_0 M_1 M_2 M_4

$g_m > g_{mb}$ to M_3

What is the relation ($\ll, <, =, >, \gg$) between c_{gs} and c_{gd} ?

$|C_{gs}| \ll |C_{gd}|$

What is the relation ($\ll, <, =, >, \gg$) between c_{sb} and c_{db} ?

$|C_{sb}| > |C_{db}|$ to M_0 M_1 M_2 M_4

$|C_{sb}| \ll |C_{db}|$ to M_3


2. AC Analysis

1) Create a new simulation configuration. Perform AC analysis (1Hz:10GHz, logarithmic, 10points/decade) to simulate gain and bandwidth.

2- Use calculator to create expressions for circuit parameters (DC gain, BW, GBW, and UGF) and export them to adexl.

```
No. of Data Rows : 101
peak1                = 4.712516e+01 at= 1.000000e+00
f3db1                = 6.717666e+05
ugf1                 = 3.156354e+07
gbw1 = 3.165711e+07
peak2                = 1.475165e+03 at= 1.000000e+00
f3db2                = 2.066319e+04
ugf2                 = 3.062239e+07
gbw2 = 3.048161e+07
```

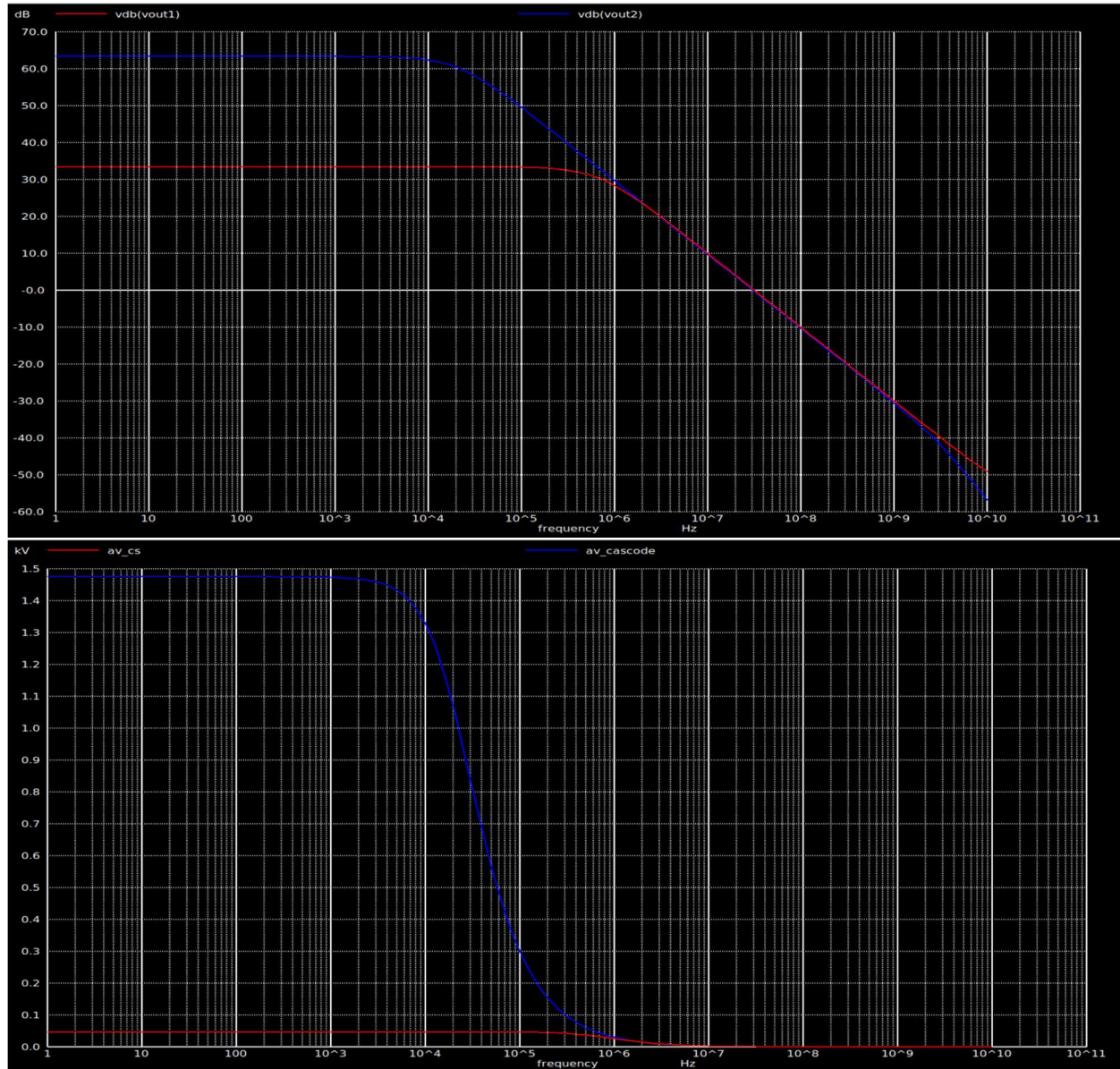3) Report the Bode plot (magnitude) of CS and cascode **appended on the same plot.**



4) Using small signal parameters from OP simulation, perform hand analysis to calculate DC gain, BW, and GBW of both circuits.


```

No. of Data Rows : 1
igain0 = 4.697477e+01
igain1 = 1.470747e+03
binary raw file "lab3.raw"
BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m_xm4.m0      m_xm2.m0      m_xm1.m0
  model      nmos_3p3.8      nmos_3p3.8      nmos_3p3.8
  id          2e-05          2e-05          2e-05
  vgs         0.90218        0.915022       0.814542
  vds         0.902172       0.4667         0.44782
  vth         0.773009       0.780565       0.682219
  vdsat       0.164456       0.167975       0.164748
  gm          0.000198406     0.000195565    0.000195901
  gds         4.5533e-06      5.70778e-06    5.51981e-06
  gmb         4.09662e-05     4.09682e-05    5.35256e-05
  cdb         -1.99264e-16       -2.05429e-16   -2.67635e-16
  cgd         2.53027e-17      2.06986e-17    1.42304e-17
  cgs         -2.36966e-15     -2.39504e-15   -2.34144e-15
  csb         -2.98496e-16       -3.05899e-16   -3.9823e-16

BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m_xm0.m0      m_xm3.m0
  model      nmos_3p3.8      nmos_3p3.10
  id          2e-05          2e-05
  vgs         0.788833       1.36286
  vds         0.888826       0.460663
  vth         0.662441       0.656113
  vdsat       0.16076       0.548263
  gm          0.000199102     4.5917e-05
  gds         4.2385e-06      1.26435e-05
  gmb         5.40445e-05     1.77984e-05
  cdb         -2.61442e-16     -8.1538e-15
  cgd         1.93885e-17     -4.44422e-15
  cgs         -2.31164e-15     -4.47538e-14
  csb         -3.91625e-16     -1.07572e-14

No. of Data Rows : 101
peak1      = 4.712516e+01 at= 1.000000e+00
f3db1      = 6.717666e+05
ugf1       = 3.156354e+07
gbw1 = 3.165711e+07
peak2      = 1.475165e+03 at= 1.000000e+00
f3db2      = 2.066319e+04
ugf2       = 3.062239e+07
gbw2 = 3.048161e+07

```

Gain

CS $A_v = g_m \cdot r_o = 50 \text{ dB}$

calculate DC $A_v = (g_{m2} + g_{mb2}) r_{o2} g_{m3} r_{o3} = 1469 \text{ dB}$

B_w

For CS: $BW = \frac{1}{(2\pi r_o C_L)} = 668.56 \text{ kHz}$

For Cascode: $BW = \frac{1}{2\pi(r_{o2} + (1 + (g_{m2} + g_{mb2})r_{o2})r_{o3}) C_L} = 20.57 \text{ KHz}$

GBW & UGF:

For CS: $GBW = UGF = A_v \cdot BW = 32.76 \text{ MHz}$

For Cascode: $GBW = UGF = A_v \cdot BW = 29.86 \text{ MHz}$

5) Report a table comparing the DC gain, BW, UGF, and GBW of both circuits from simulation and hand analysis.

Analysis	Analytical			Simulation		
Quantity	Gain	BW	GBW & UGF	Gain	BW	GBW & UGF
CS	50 dB	668.5 kHz	32.7MHz	47.1dB	671.76k	31.6M
Cascode	1469 dB	20.57KHZ	29.86MHz	1475dB	20.66k	30.48M

6) Comment on the results


The bandwidth of the cascode amplifier is much less than the conventional amplifier, but the gain of the cascode amplifier is much greater than the conventional amplifier. This means that almost the same bandwidth is achieved. It is a mixture of gain and bandwidth because more weight increases the bandwidth and vice versa.

Part 3: “Optional” Cascode for BW

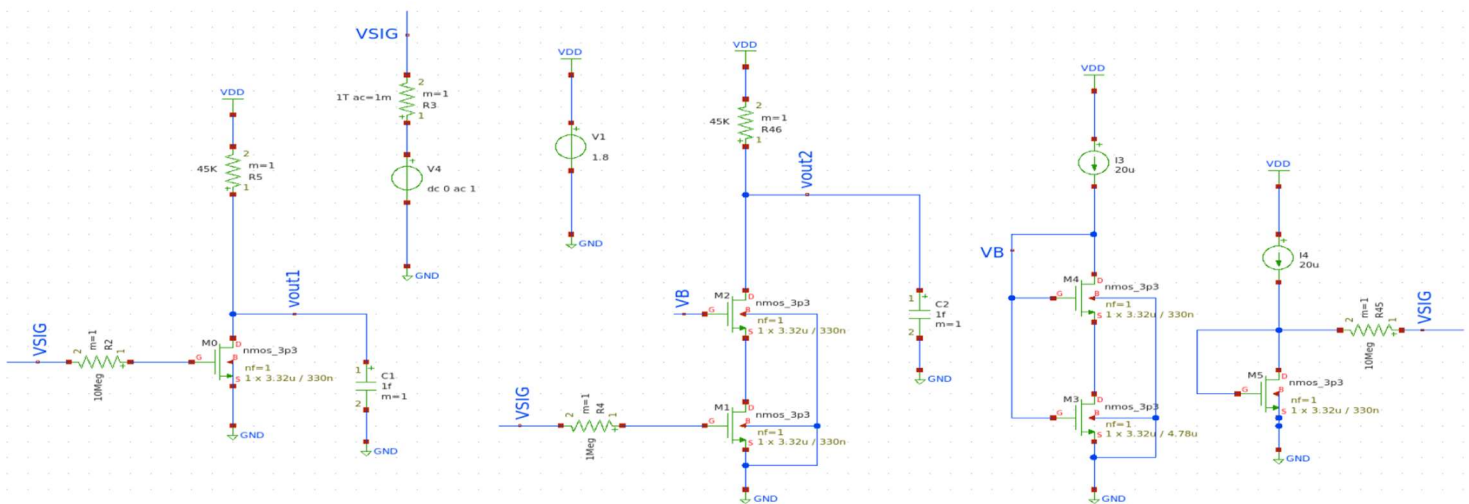1. OP Analysis

$$V_{DD} = V_D + V_{RD} = V_D + I_D \cdot R_D$$

$$1.8 = 0.9 + 20\mu \cdot R_D, R_D = 45K$$




```

No. of Data Rows : 1
igain0 = 8.579451e+00
igain1 = 1.978884e-03
binary raw file "lab3.raw"
BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.xm5.m0      m.xm4.m0      m.xm2.m0
model      nmos_3p3.8      nmos_3p3.8      nmos_3p3.8
id          2e-05      2e-05      1.905e-05
vgs         0.802474      0.894545      0.901974
vds         0.802467      0.894538      0.486536
vth         0.674905      0.765476      0.772919
vdsat       0.161587      0.164358      0.164304
gm          0.000198572      0.000198527      0.000190654
gds         4.33782e-06      4.56545e-06      5.3774e-06
gmbs        5.39751e-05      4.09315e-05      3.97485e-05
cdb         -2.6236e-16      -1.9898e-16      -2.0279e-16
cgd         1.92066e-17      2.53207e-17      2.1491e-17
cgs         -2.31723e-15      -2.36962e-15      -2.37561e-15
csb         -3.92848e-16      -2.98062e-16      -3.0225e-16

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.xm1.m0      m.xm0.m0      m.xm3.m0
model      nmos_3p3.8      nmos_3p3.8      nmos_3p3.10
id          1.905e-05      2.12339e-05      2e-05
vgs         0.802467      0.802466      1.35817
vds         0.456183      0.844457      0.463611
vth         0.675351      0.669362      0.652517
vdsat       0.16125      0.165253      0.547433
gm          0.000190862      0.000205641      4.62501e-05
gds         5.2452e-06      4.45735e-06      1.21762e-05
gmbs        5.2123e-05      5.58771e-05      1.78975e-05
cdb         -2.65584e-16      -2.6402e-16      -8.11294e-15
cgd         1.4666e-17      1.94804e-17      -4.27754e-15
cgs         -2.32203e-15      -2.33691e-15      -4.47847e-14
csb         -3.95403e-16      -3.95406e-16      -1.07428e-14



```

4) Check that all transistors operate in saturation. Does any transistor operate in triode? Why?

all transistors in saturation but M3 in triode

saturation $V_{DS} > V_{dsat} * 1.2$

2. AC Analysis

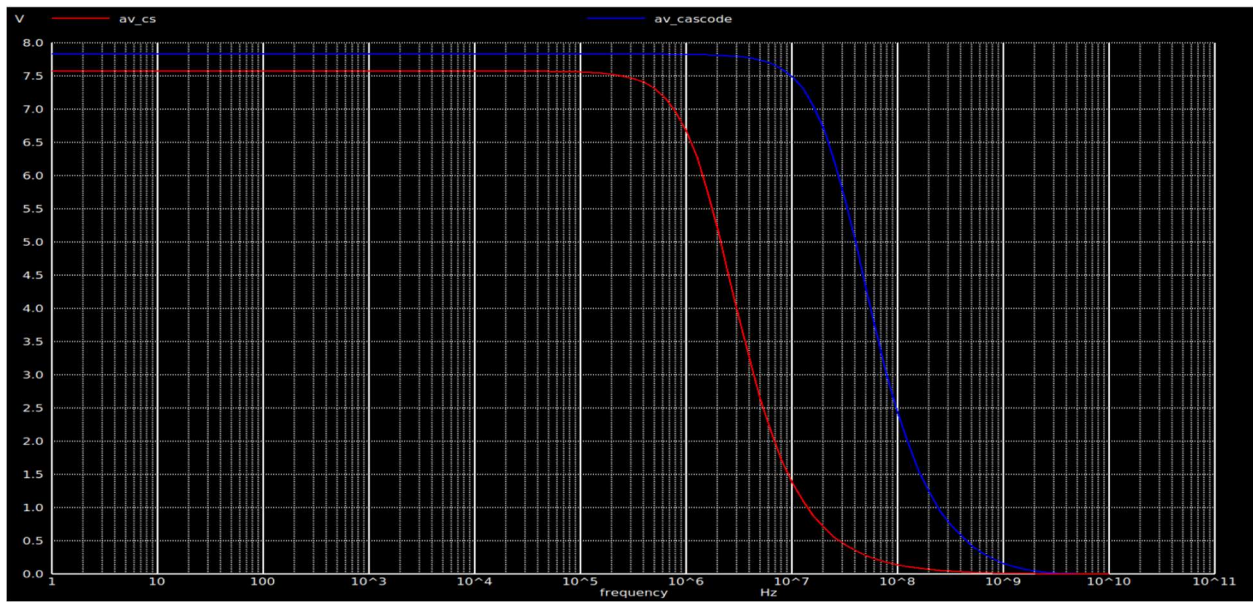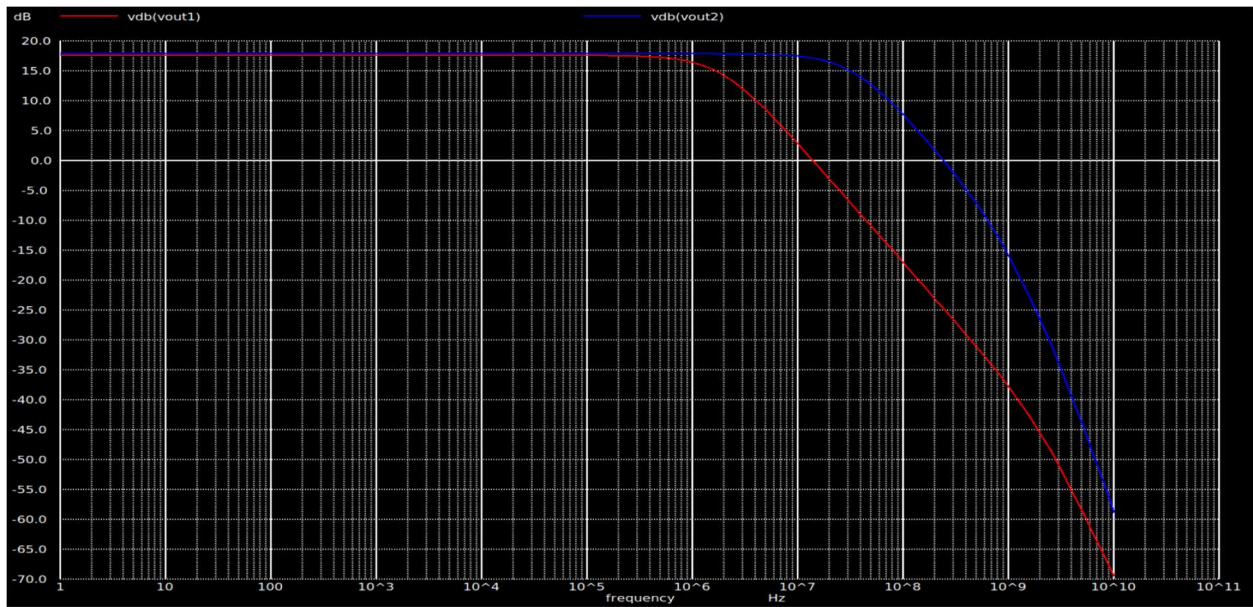

```

No. of Data Rows : 101
peak1           = 7.572658e+00 at= 1.000000e+00
f3db1           = 1.861416e+06
ugf1            = 1.411224e+07
gbw1 = 1.409587e+07
peak2           = 7.830699e+00 at= 1.000000e+00
f3db2           = 3.289306e+07
ugf2            = 2.429207e+08
gbw2 = 2.576226e+08

```

Analysis	Analytical			Simulation		
Quantity	Gain	BW	GBW & UGF	Gain	BW	GBW & UGF
CS	7.46dB	1.78MHZ	13.69MHz	7.57dB	1.86M	14.11M
Cascode	7.69 dB	3.19MHZ	241.5MHz	7.83dB	3.28M	242.9M

The comment

The bandwidth of the cascode amplifier is significantly lower than that of a conventional amplifier, but the gain of the cascode amplifier is much higher than that of the conventional amplifier. This results in nearly the same overall bandwidth. It is a balance between gain and bandwidth, where increasing one tends to decrease the other, and vice versa.