

Analog IC Design – Xschem and Master Micro Tools

Lab 06

Differential Amplifier

Part 1: Differential Amplifier Design

Parameter	
Supply (V_{DD})	1.8V
Bias current (I_{SS})	40 μ A
Differential gain	8
CM output level ¹	$V_{DD}/3$
Load capacitance	1pF

$$I_D = 20\mu A.$$

$$\text{CM output level1} = V_{DD}/3 = 1.8/3 = 0.6 \text{ v}$$



$$R_D = (2V_{out-CM}) / I_{SS} = 1.2 / 40\mu = 30k$$

$$\text{Differential gain} = 8$$



$$V_* = 1.82 * I_D * R_D / |A_v| = (1.82 * 20\mu * 30k) / 8 = 136.5 \text{ mv}$$

ID	20u	3	L	350n	16	gm	286.7u
Vstar	136m	4	W	30.79u	17	gmb	93.21u
ro	30*10k	5	VGS	939.3m	18	gds	3.193u
VDS	0.9	6	VDS	900m	19	ro	313.2k
VSB	0.3	7	VSB	300m	20	VTH	870.2m
		8	gm/ID	14.33	21	VDSAT	121.4m
		9	Vstar	139.5m	22	cgg	41.72f
					23	cgs	29.49f
					24	cgd	4.667f

ID	20u
Vstar	100m:1m:200m
/ID*100	2
VDS	0.3
VSB	0

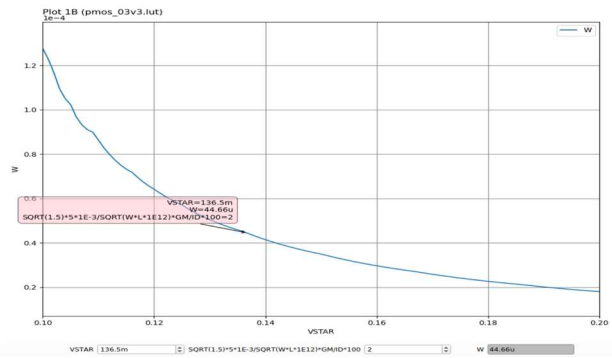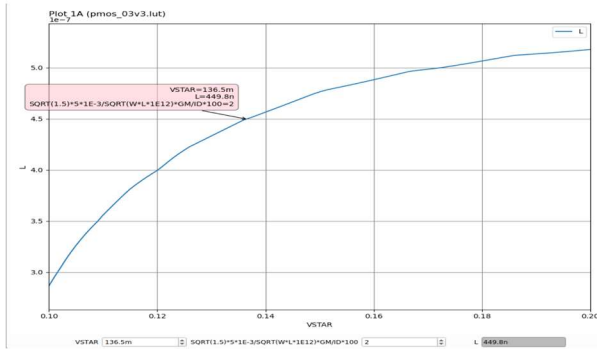


L1= 449.8n W1=44.66u

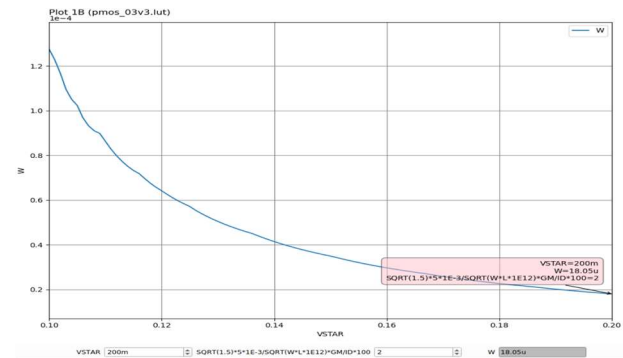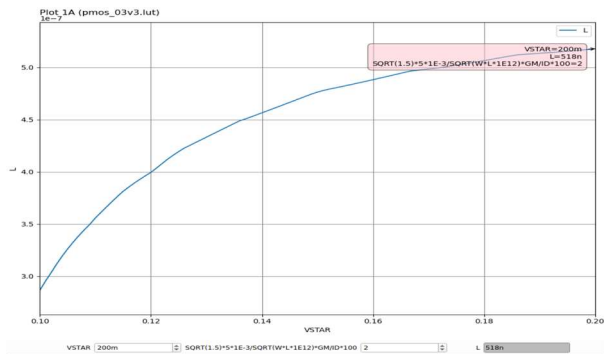

L2= 518n W2=18u

$$VICM = \min + \max / 2 = 560mv$$

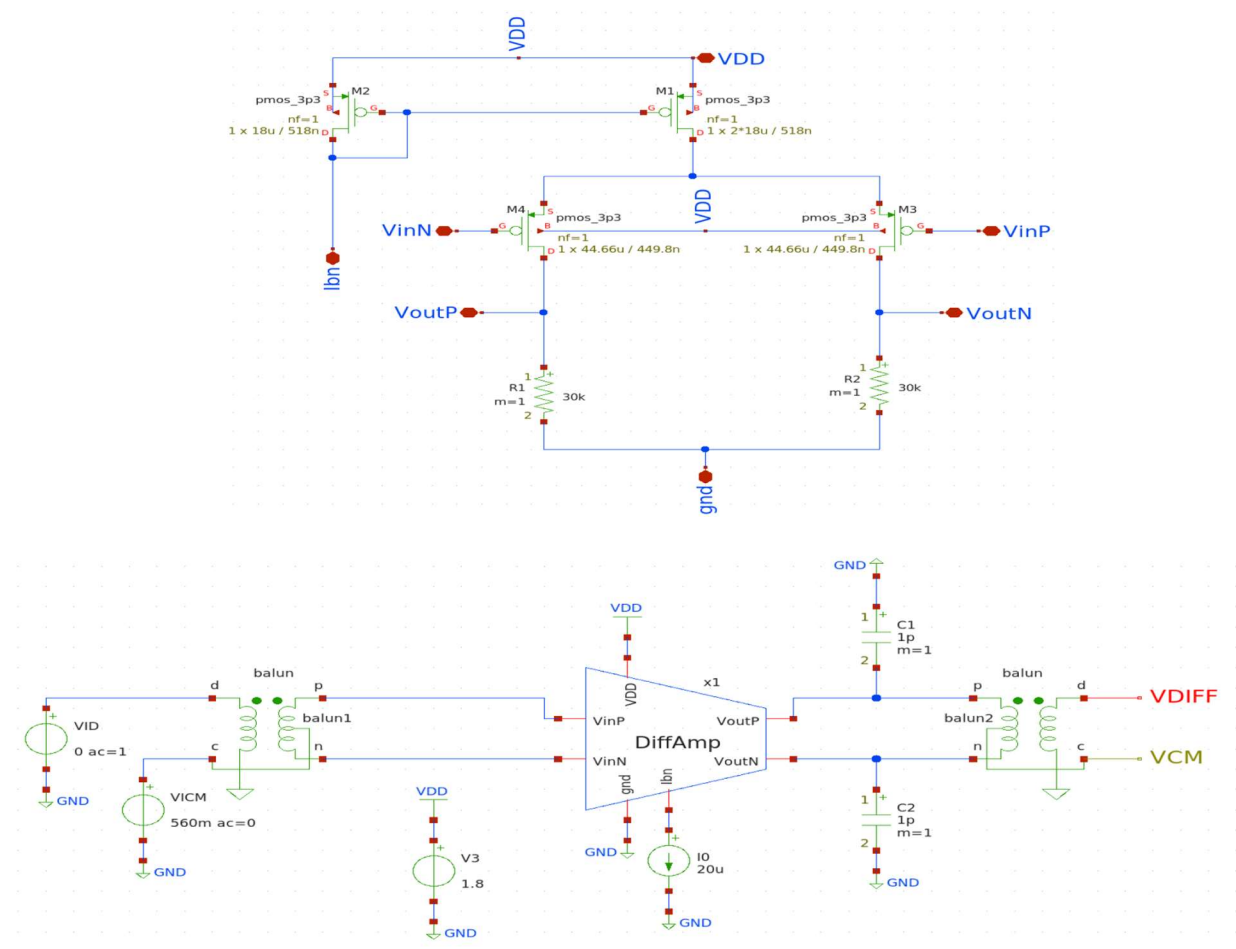Part 2: Differential Amplifier Simulation



1) OP simulation.

```

io. of Data Rows : 1
BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m_x1.xm3.m0      m_x1.xm4.m0      m_x1.xm2.m0
model       pmos_3p3.12     pmos_3p3.12     pmos_3p3.13
id          1.90244e-05     1.97623e-05     2e-05
vgs         0.958952        0.958952        0.941906
vds         0.948218        0.926082        0.941905
vdsat       0.111061        0.112679        0.166402
vth         0.899158        0.896616        0.790984
gm          0.00028764       0.000295671     0.000205003
gds         1.53187e-06      1.59936e-06     1.01315e-06
gmbs        0.000106251     0.000109225     9.17836e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m_x1.xm1.m0
model       pmos_3p3.13
id          3.87867e-05
vgs         0.941906
vds         0.281045
vdsat       0.167548
vth         0.789436
gm          0.000392408
gds         6.97932e-06
gmbs        0.000175832
    
```

Check that all transistors operate in saturation.

All Transistors operate in saturation.

2) Diff small signal ccs:

```
No. of Data Rows : 101  
gain          = 8.113316e+00 at= 1.000000e+00  
bw            = 5.368121e+06  
binary raw file "lab6_ac.raw"
```

Analytical solution:

$$BW = 1 / (2\pi (RD||ro) * CL) = 5.81 \text{ MHz}$$

$$\text{Gain} = gm(RD||ro) = 7.84 = 17.89 \text{ dB}$$

	Analytical	Simulation
BW	5.81 MHz	5.36M
GAIN	7.84	8.11

3) CM small signal ccs:




```
No. of Data Rows : 101  
cmgain        = 6.132381e-05 at= 1.258925e+01  
binary raw file "lab6_ac.raw"
```


Every time I do a simulation the result changes a lot.

$$AVCM = \frac{gm(RD||ro)}{1+2gmRSS} = 0.67$$



	Analytical	Simulation
CM, GAIN	0.67	0.613

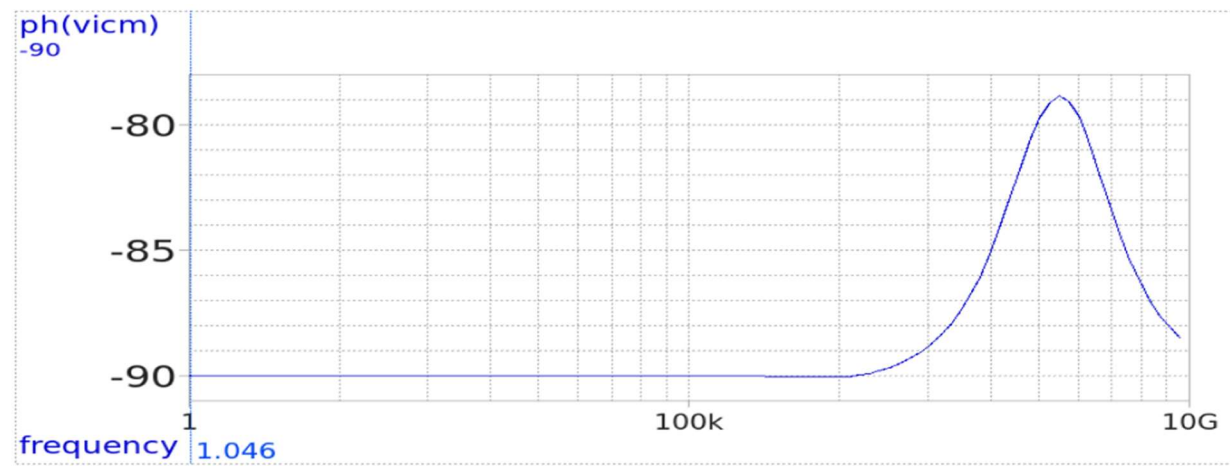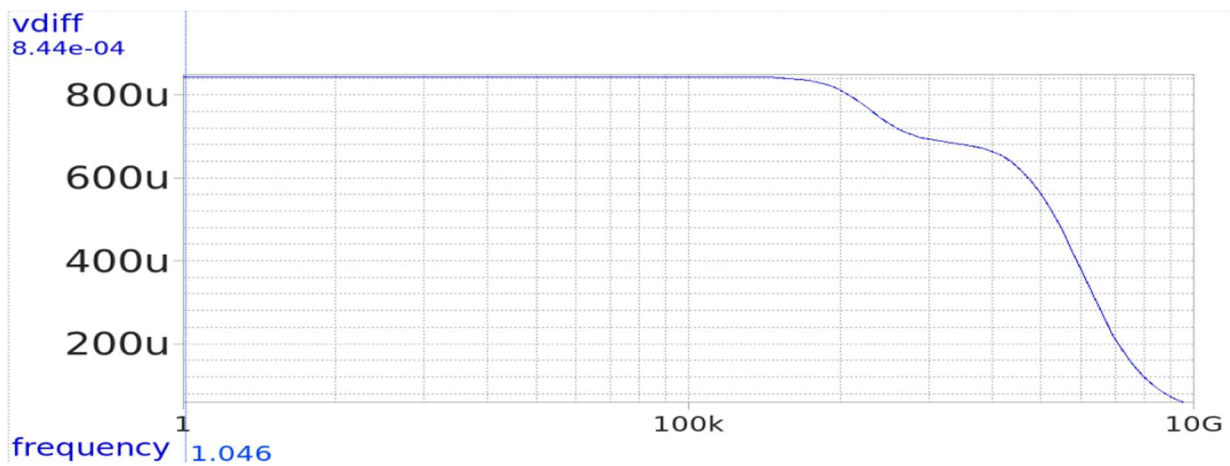
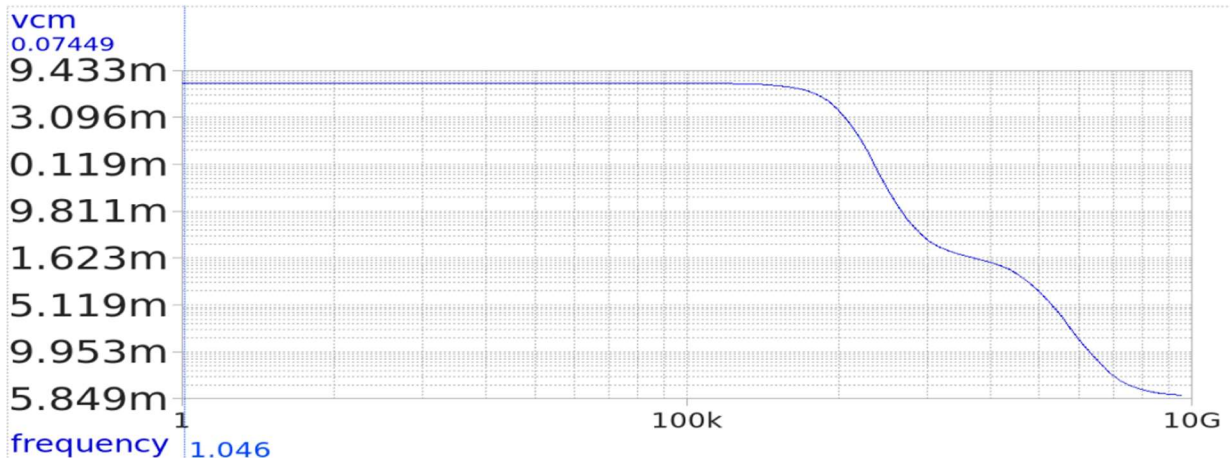
Yes, it is less than 1 because it is degraded by a large resistance $2RSS$.



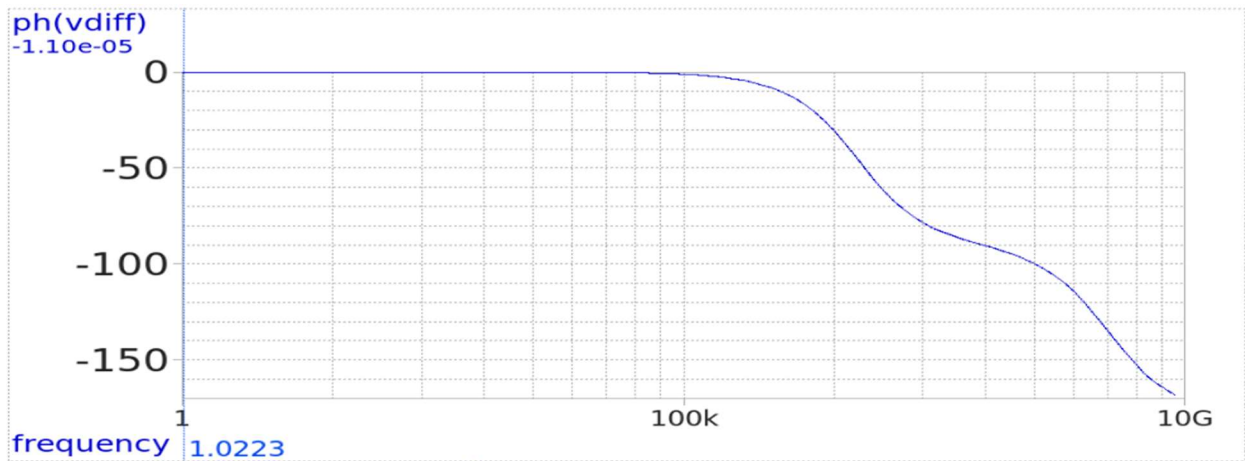
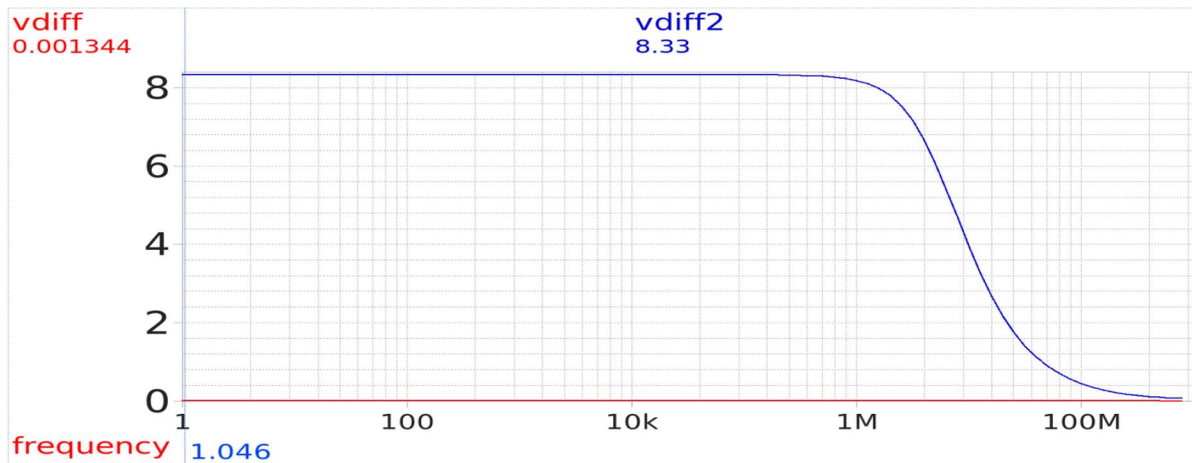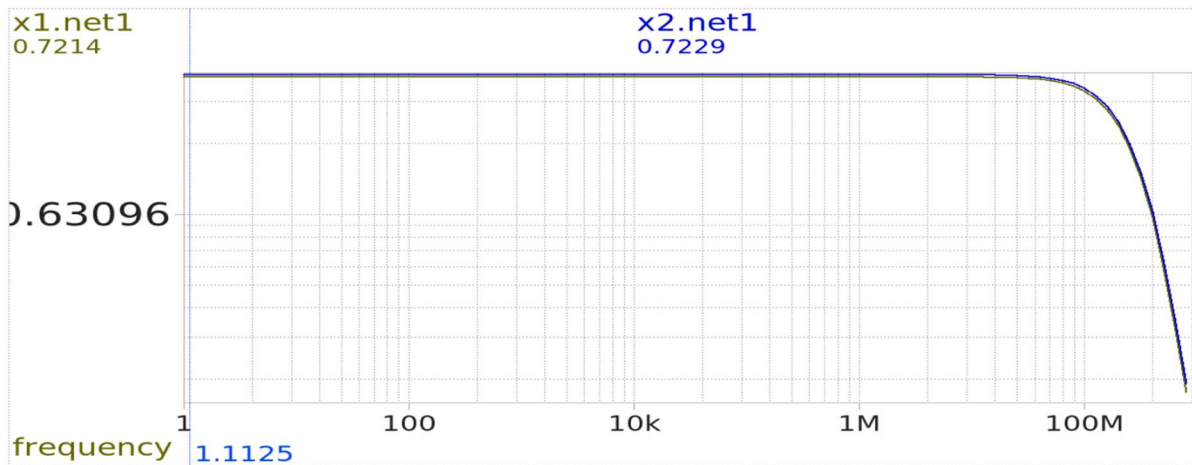
```
No. of Data Rows : 91
cmgain      = 7.008331e-02 at= 1.000000e+00
to=1meg: no such command available in ngspice
diffgain    = 8.329921e+00 at= 1.000000e+00
to=1meg: no such command available in ngspice
cmrr_val = 1.188564e+02
binary raw file "lab6_ac_CM.raw"
```



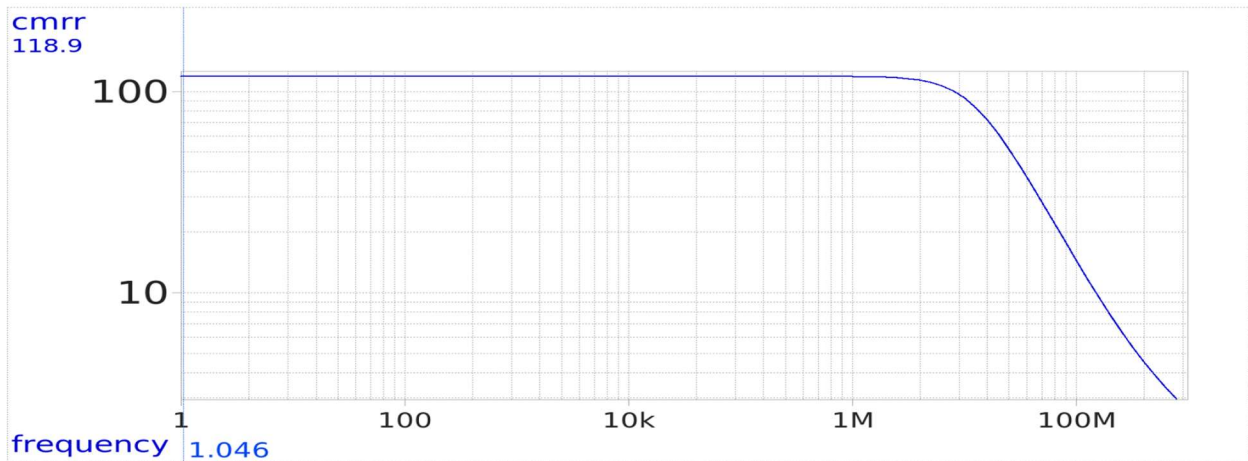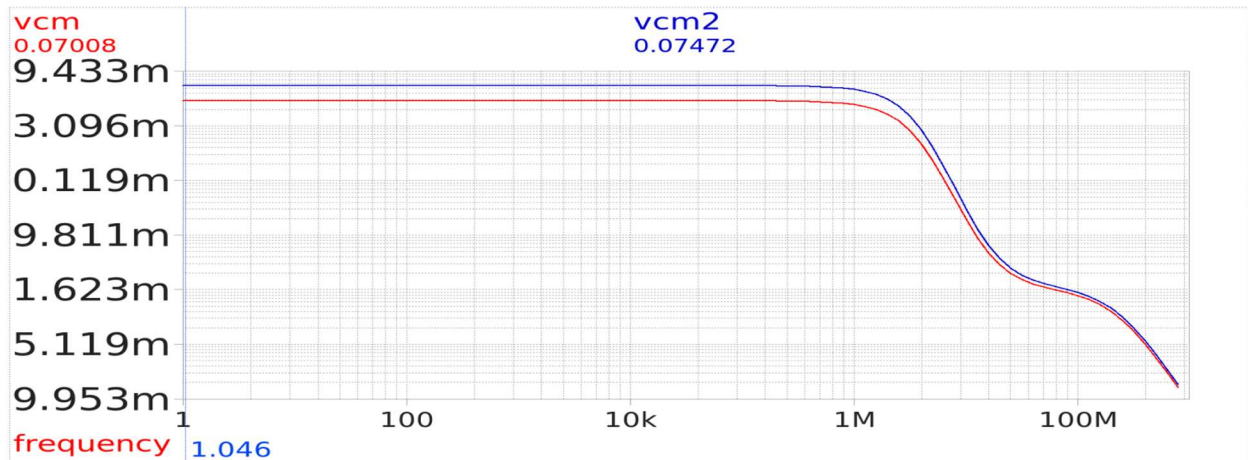



Initially, AV_{CM} decreases because R_D is converted with C_L which reduces the impedance and gain, at higher frequencies, AV_{CM} increases slightly which means that R_{SS} is converted with the capacitance of M_0 and M_3 which reduces the total impedance.

$$CMRR = V_{diff}/v_{cm}$$

CMRR varies with the variations of V_{CM} at high frequencies.

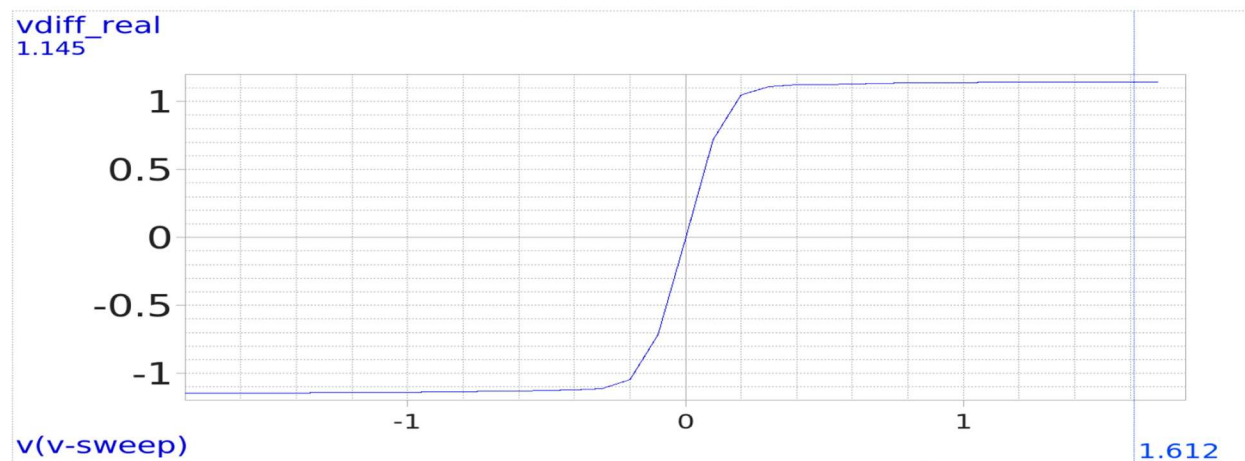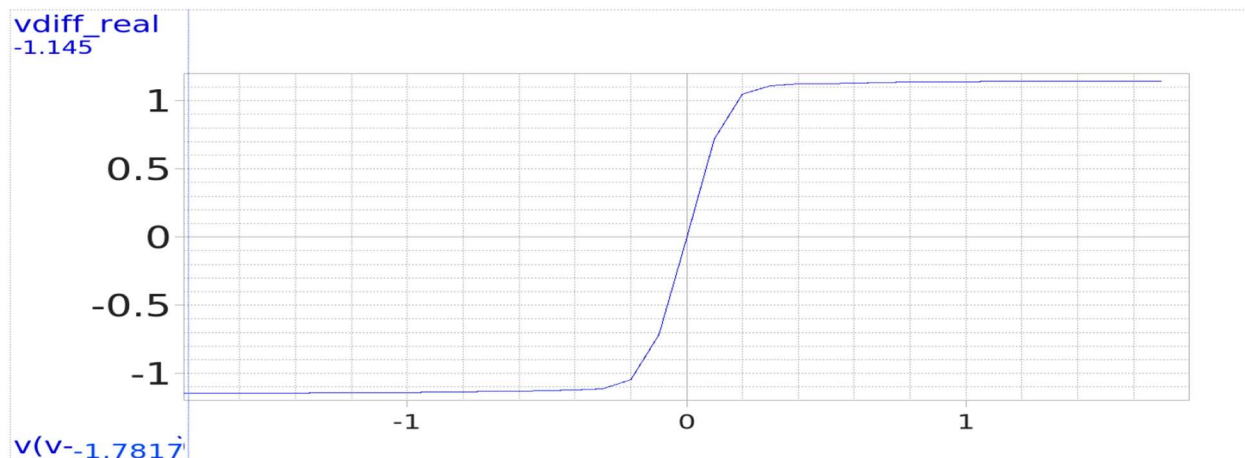4) Diff large signal ccs:

Report diff large signal ccs (V_{ODIFF} vs V_{IDIFF}). Compare the extreme values with hand analysis in a table.



- At $V_{diff} \gg 0$, $V_{diff} = I_{SS} * R_D = 1.2V$
- At $V_{diff} \ll 0$, $V_{diff} = -I_{SS} * R_D = -1.2V$

	Analytical	Simulation
$V_{diff} \gg 0$	1.2V	1.145V



$V_{diff} \ll 0$	-1.2V	-1.145V
------------------	-------	---------



5) CM large signal ccs (GBW vs Vicm):

```

binary raw file "Lab6_param.raw"
vicmax = 7.500000e-01
vicmin = -4.700000e-01
ngspice 1 -> █

```

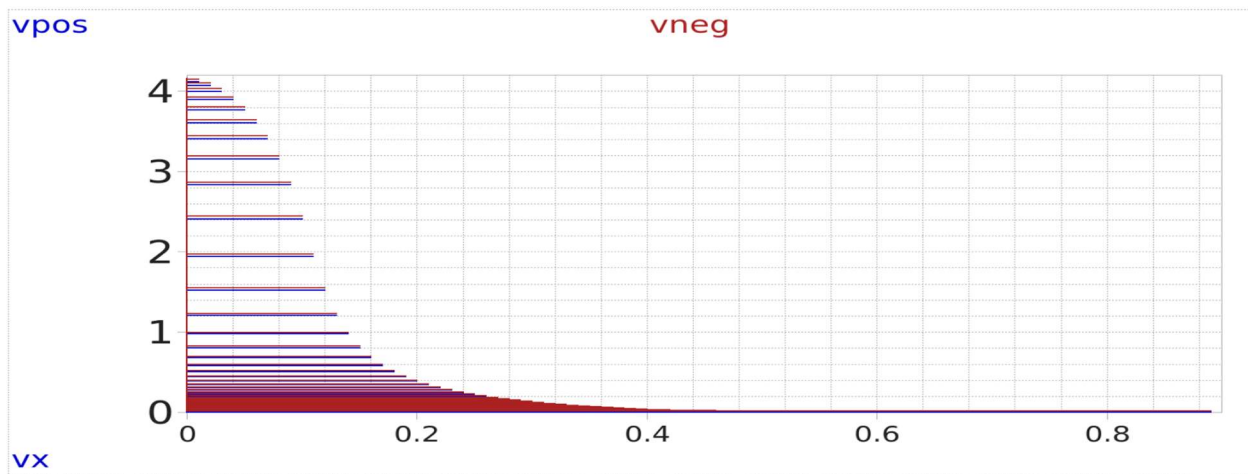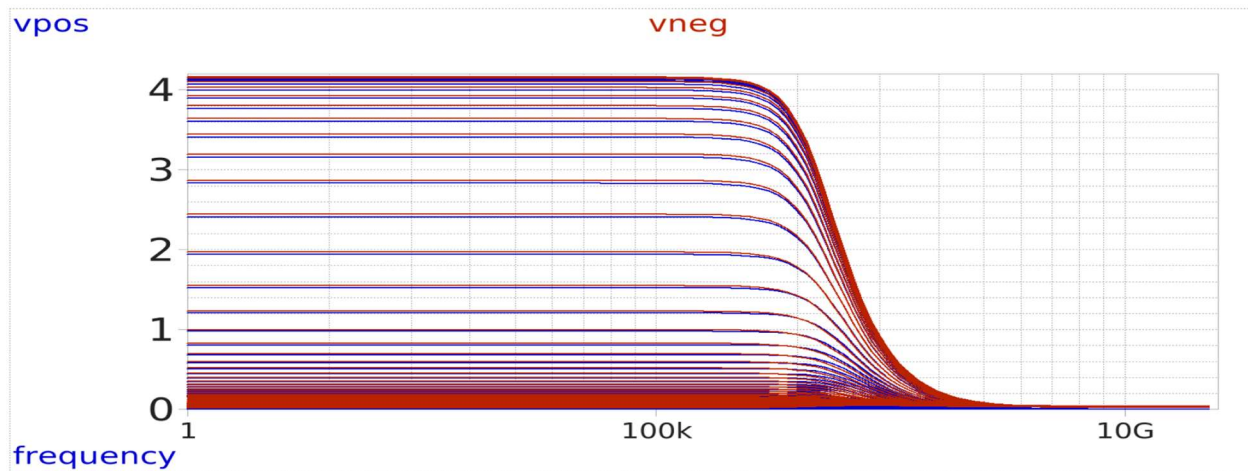

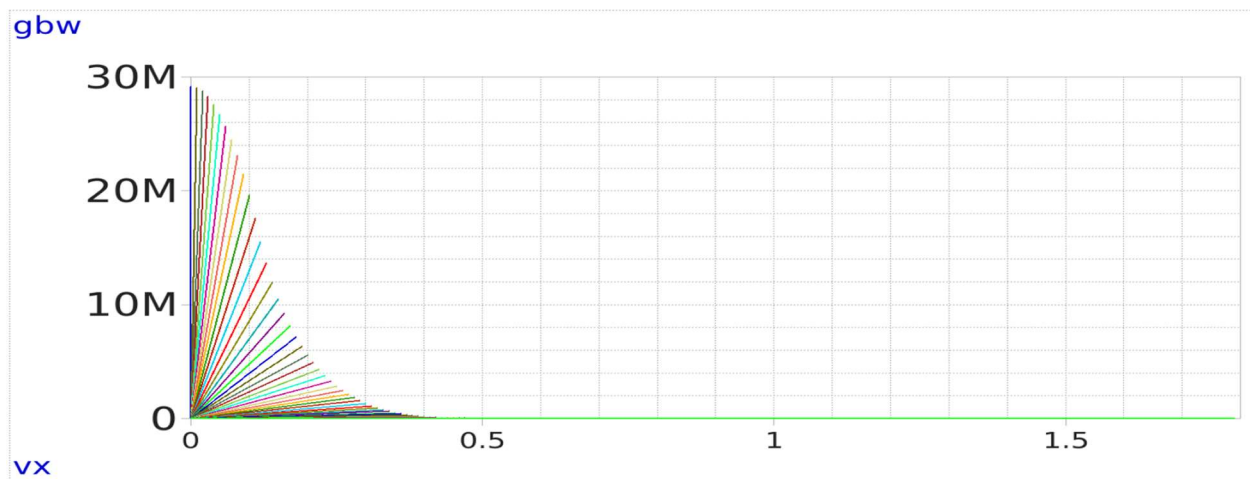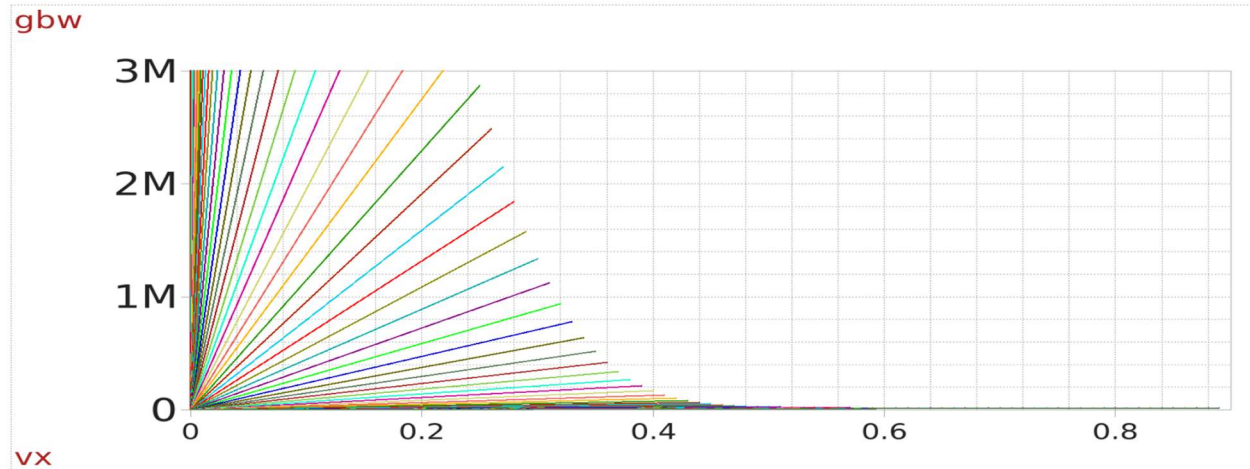

$$CMIR = V_{max} - V_{min} = (7.5e-1) - (-4.7e-1) = 1.22v$$

$$(VDD - V_{ov} - V_{GS}) > V_{icm} > ([ISS/2] * R_D - V_{TH})$$

$$0.808 > V_{icm} > -0.27$$

	Analytical	Simulation
VMIR	1.07V	1.22v


Wide Swing_ Current Mirror

LUT	nmos 03v3	?
Corner	TT	<input type="checkbox"/> All ?
Temp (°C)	27.0	<input type="checkbox"/> All ?
Frequency	1	?
Stack	1	?
ID	20u	?
Vstar	200m	?
L	1u	?
VDS		?
VSB	0	?

Results:		
	Name	TT-27.0
1	ID	20u
2	IG	N/A
3	L	1u
4	W	9.04u
5	VGS	829.4m
6	VDS	

LUT	pmos 03v3	?
Corner	TT <input type="checkbox"/> All	?
Temp (°C)	27.0 <input type="checkbox"/> All	?
Frequency	1	?
Stack	1	?
ID	20u	?
Vstar	200m	?
L	1u	?
VDS		?
VSB	0	?

Name		TT-27.0
1	ID	20u
2	IG	N/A
3	L	1u
4	W	38.12u
5	VGS	942.1m
6	VDS	

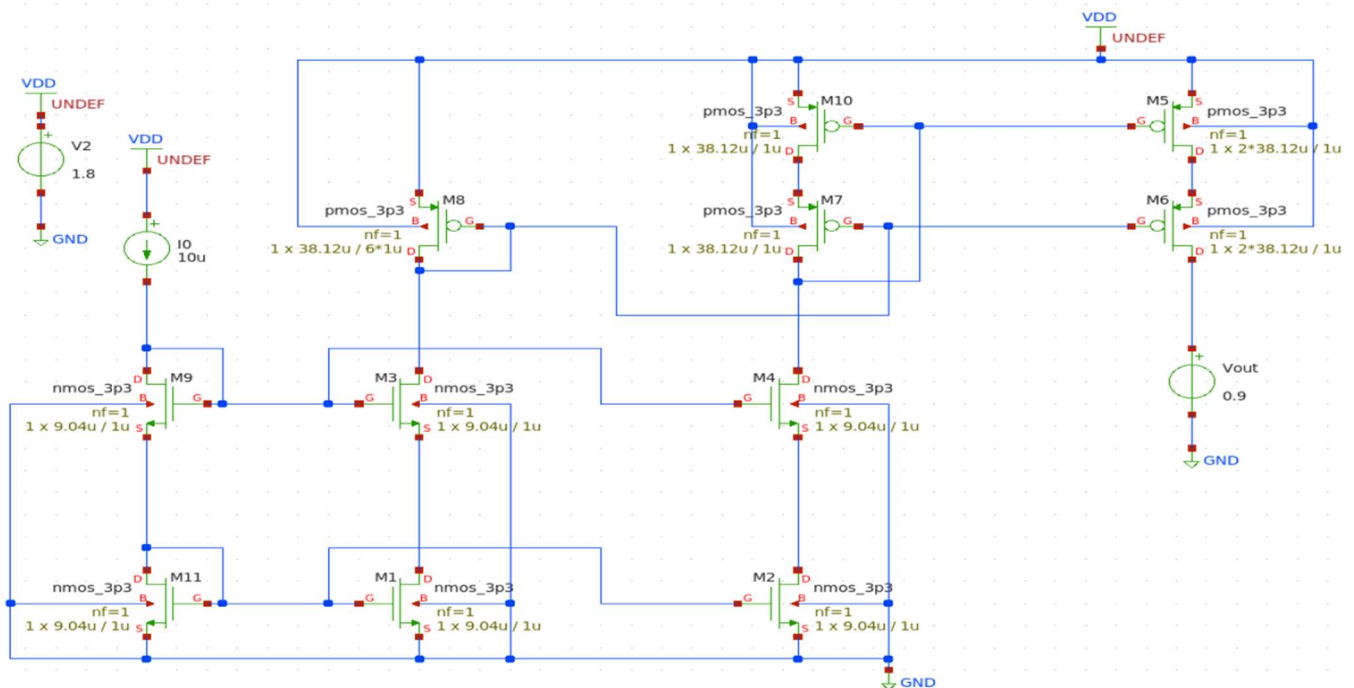

1. OP Analysis

lo. of Data Rows : 1

BSIM4v5: Berkeley Short Channel IGFET Model-4

device	m.xm8.m0	m.xm7.m0	m.xm6.m0
model	pmos_3p3.14	pmos_3p3.13	pmos_3p3.13
id	9.3927e-06	9.38471e-06	1.92893e-05
vgs	1.09229	0.94625	0.946199
vds	1.09229	0.738716	0.753905
vdsat	0.244223	0.116442	0.117704
vth	0.768938	0.852158	0.850091
gm	5.34798e-05	0.000124199	0.000253065
gds	3.47672e-08	2.6492e-07	5.3612e-07
gmbs	2.61796e-05	5.43524e-05	0.000110739

BSIM4v5: Berkeley Short Channel IGFET Model-4

device	m.xm5.m0	m.xm10.m0	m.xm11.m0
model	pmos_3p3.13	pmos_3p3.13	nmos_3p3.9
id	1.92893e-05	9.38471e-06	1e-05
vgs	0.88476	0.88476	0.769232
vds	0.146094	0.146043	0.76923
vdsat	0.117489	0.116163	0.128757
vth	0.783634	0.785783	0.684503
gm	0.000240692	0.000118348	0.000130185
gds	1.57685e-05	7.4542e-06	3.95678e-07
gmbs	0.000114154	5.61279e-05	4.98495e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4

device	m.xm9.m0	m.xm4.m0	m.xm3.m0
model	nmos_3p3.9	nmos_3p3.9	nmos_3p3.9
id	1e-05	9.38471e-06	9.3927e-06
vgs	1.02103	1.02354	1.11827
vds	1.02102	0.148517	0.0357127
vdsat	0.135345	0.135452	0.227753
vth	0.935741	0.938082	0.910949
gm	0.000130652	0.000118647	4.55458e-05
gds	3.25778e-07	8.44878e-06	0.000239683
gmbs	3.67723e-05	3.3431e-05	1.36062e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4

device	m.xm2.m0	m.xm1.m0
model	nmos_3p3.9	nmos_3p3.9
id	9.38471e-06	9.3927e-06
vgs	0.769232	0.769232
vds	0.766717	0.671988
vdsat	0.12562	0.125851
vth	0.689268	0.688914
gm	0.000124736	0.000124781
gds	3.78272e-07	3.96337e-07
gmbs	4.77682e-05	4.77808e-05

2. DC Sweep (I_{out} vs V_{OUT})

